

Materials:

Libraries	Adafruit Neopixel
Light	Neopixel Stick with 8 RGB WS2812 LEDs
Board	Arduino UNO

+Portable battery

+ breadboard

3 wires are needed, 5V, GND, and one for DIN

5V from the light strip is plugged into the 5V from the arduino

GND from the light strip is plugged into the GND for arduino

DIN from the light strip is plugged into signal pin #6 on the arduino

